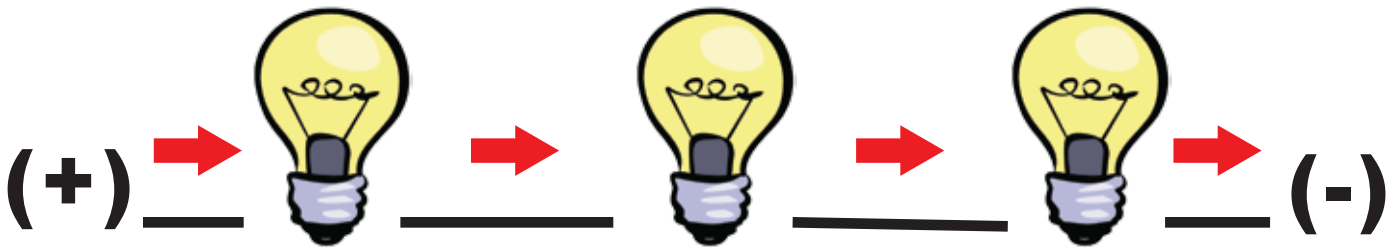


“How to figure the resistance in a Series Circuit”

Circuits in Series

Add individual resistances together to determine the total resistance. (3 circuits)

$$R = R_1 + R_2 + R_3$$



$$\mathbf{R = R_1 + R_2 + R_3}$$

